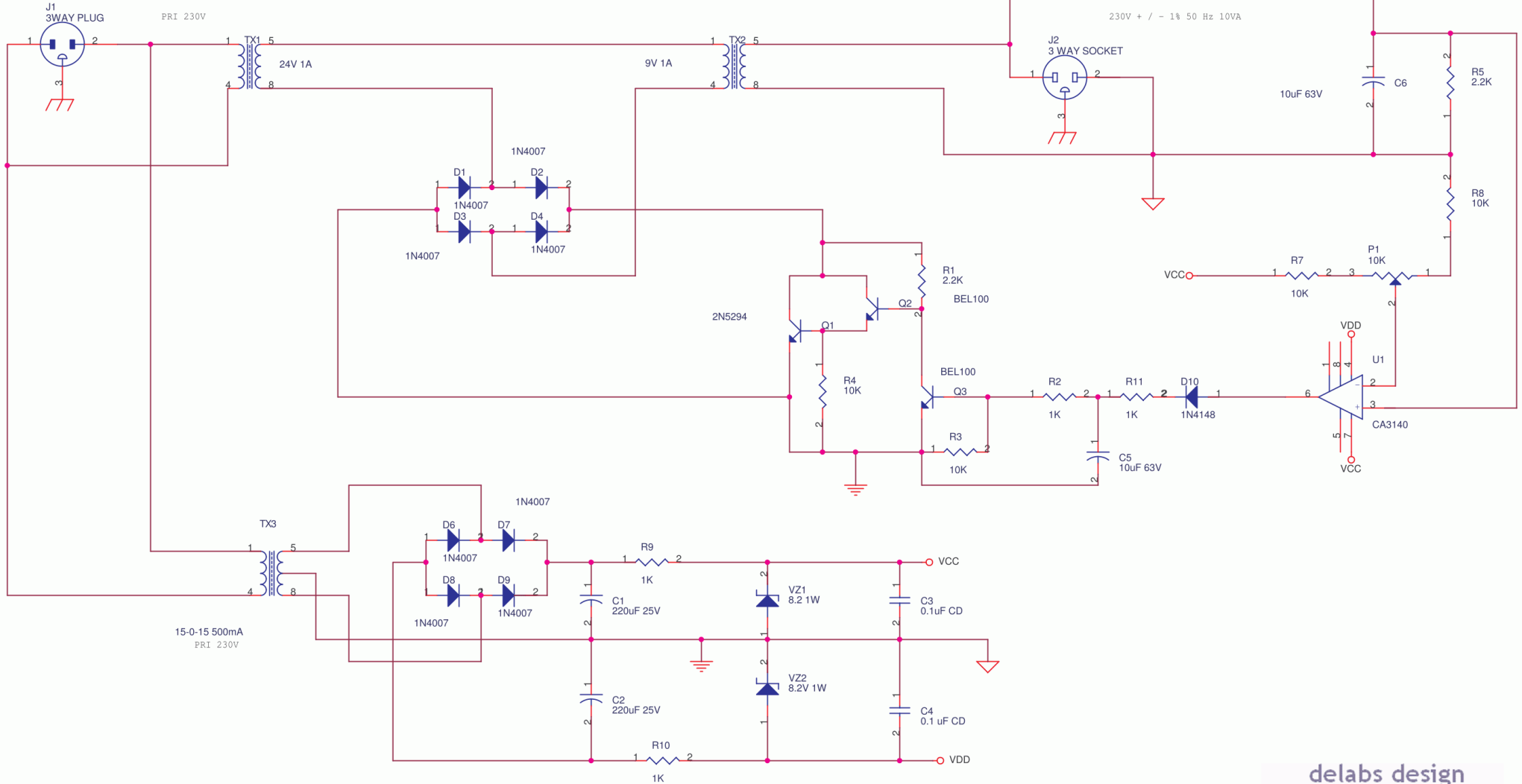


230V + / - 30% 50 Hz



CIRCUITS PROVIDED BY ANANTHA NARAYAN DELABS ARE FOR EDUCATIONAL PURPOSE ONLY.
 THE CIRCUITS ARE NOT PROVEN WORKING DESIGNS BUT CAN BE EXPERIMENTED UPON.
 THE USER OF THIS CIRCUIT WILL EXPERIMENT/APPLY/BUILD PROJECTS AT HIS OWN RISK.

delabs design
 delabs-circuits.com
 delabs.net
 Intellectual Property